




- Notes :
1. All questions are compulsory and carry equal marks.
 2. Draw neat and well labelled diagram wherever necessary.
 3. Use of log table / calculator is allowed.

EITHER:

1. a) Explain function of transistor as an amplifier. Why is it generally beneficial for an amplifier to have a high input resistance ? Explain Determine the input resistance of the amplifier when an input voltage of the source, V_s to provide an amplifier input voltage V_i of 0.25V. When the internal resistance of the source is 50Ω ? **10**

OR

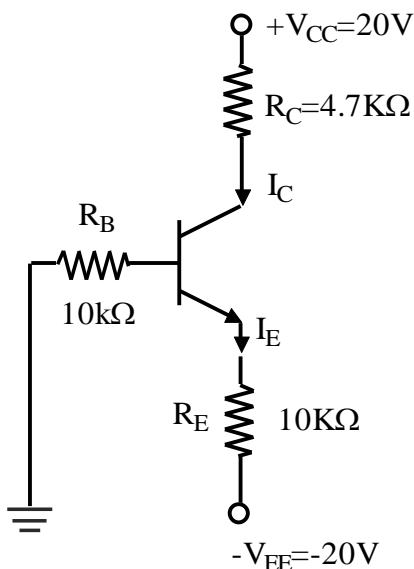- b) State various methods used for transistor biasing. Explain any one of them. For the emitter bias circuit shown below, find operating point Q for $\beta = 85$ and $V_{BE} = 0.7V$. **10**



EITHER:

2. a) Draw circuit diagram of two stages transformers coupled amplifier and explain its frequency response. **10**

A loudspeaker has a resistance of 10Ω and is coupled through transformer to the output stage of an amplifier. If the output impedance of amplifier is $1k\Omega$, Find the turn ratio of the transformer so that maximum power is transferred to the loudspeaker.

OR

- b) Derive an expression for voltage amplification of RC coupled amplifier for low frequency range. **10**

Show that lower cut off frequency is given by.

$$f_1 = \frac{1}{2\pi c(hie + R_L)}$$

EITHER:

3. a) Draw block diagram of operational amplifier. Explain why a difference amplifier is used as a building block for OP-AMP. **10**
State at least four characteristics of ideal OP-AMP.

OR

- b) Draw OP-AMP symbol with proper labels. Explain the following parameters of OP-AMP; **10**
- Differential mode gain (A_d),
 - Common mode gain (A_c),
 - Input bias current (I_B) and
 - Input offset voltage (V_{IO}).

EITHER:

4. a) What is Schmitt trigger? **10**
Explain UTP, LTP and hysteresis of Schmitt trigger. State its advantages over usual comparator.

OR

- b) Explain the concept of virtual ground. Derive the formula for output voltage of inverting amplifier, using OP-AMP. Inverting amplifier uses $20k\Omega$ input series resistor and $80k\Omega$ feedback resistor. If output is $-4V$, find the input voltage. **10**

5. a) Define h-parameters of a transistor in CE mode. **2½**
- b) State types of distortion in amplifier. Explain any one of them. **2½**
- c) Find slew rate of OP-AMP if the output voltage of OP-AMP changes from $-12V$ to $12V$ in $4 \mu\text{sec}$. **2½**
- d) Using OP-AMP, design a circuit that represents the following equations. **2½**
 $V_0 = A_2 V_2 - A_1 V_1$.
